

Principles of Analog In-Circuit Testing

By Anthony J. Suto, Teradyne, December 2012

In-circuit test (ICT) has been instrumental in identifying manufacturing process defects and component defects on countless varieties of populated printed circuit board (PCB) assemblies for more than 40 years. ICT operates by gaining direct electrical access to the board under test through a bed-of-nails fixture and other limited-access techniques including IEEE 1149.1 boundary-scan and IEEE 1149.8.1 powered opens. When performing electrical tests, each active and passive component typically is isolated from other surrounding components and tested on an individual basis.

Passive components including resistors, capacitors, inductors, and circuit-protection devices compose the highest percentage of all devices that are populated on today's PCB assemblies. However, the successful isolation and testing of these components during ICT is perhaps the most challenging and the least understood of all modern-day validation practices.

Measurement Basics

There are two common methods used to measure the resistance, inductance, and capacitance (RLC) of a device. The first is to force an AC current and measure the AC voltage drop across the component. A second method is to force an AC voltage across the component and measure the resultant AC current flowing through the impedance.

Any surrounding components electrically connected to the DUT are neutralized from affecting the measurement by a process known as guarding, which can be either passive or active in nature. In addition, the AC stimulus voltage typically is made low enough in amplitude to avoid accidentally turning on integrated circuit P-N junctions that may be attached to the DUT.¹

The voltage and current measurement data typically is created from a discrete time digitization of the two continuous time waveforms in a phase coherent manner. This results in two data vectors that then are numerically operated upon to extract the impedance value.

The preferred ICT metrology, shown in **Figure 1**, uses a voltage source as a stimulus generator (V_S) and a transimpedance amplifier or a virtual ground current meter to detect the current (I_X) that flows through the unknown device (Z_X). The source voltage and device current are both complex numerical values denoted in either Cartesian form ($V = A + jB$) or in polar form ($V = |V| e^{j\theta}$).

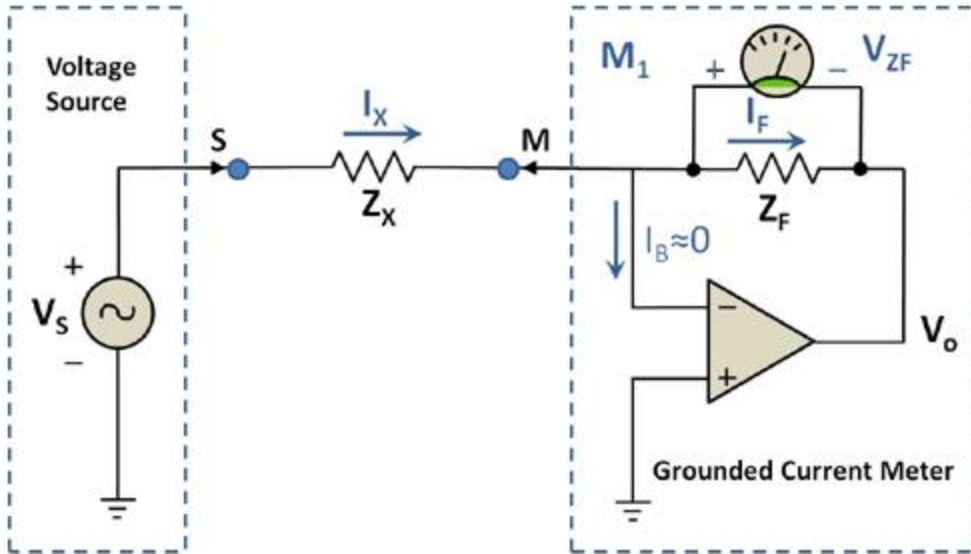


Figure 1. Simplified DUT Impedance Measurement with Grounded Current Meter

The calculated component impedance is the quotient of the complex voltage impressed across the device divided by the complex device current. Impedance is a complex value that changes as a function of the applied test frequency.

Again, referring to Figure 1, if the op-amp has negligible bias current ($I_B \approx 0$) into the negative input terminal, then all of the current flowing through the unknown impedance (I_x) also will flow through the op-amp feedback impedance Z_F , making I_x equal to I_F . Additionally, the op-amp differential input voltage ($V_+ - V_-$) is approximately equal to the output voltage V_o divided by the op-amp open-loop gain A_{V0} , which typically is a very large number at lower frequencies.

If the op-amp output voltage is limited to ± 10 V and $A_{V0} = 2 \times 10^6$ V/V, then the maximum voltage across ($V_+ - V_-$) will be only ± 5 μ V, thereby making the negative input terminal at a virtual ground potential. Finally, the output voltage V_o and the voltage across the feedback impedance can be described as follows:

$$V_o = - \left[\frac{V_s \times Z_F}{Z_x} \right] = - V_{Z_F} \quad (1)$$

Knowing the stimulus voltage amplitude V_s , the value of Z_F and the voltage V_{Z_F} across Z_F allows you to readily calculate the complex value of the unknown component:

$$Z_x = \frac{(V_s | e^{j\theta_{V_s}})}{(I_x | e^{j\theta_{I_x}})} = \frac{(V_s | e^{j\theta_{V_s}})}{(V_{Z_F} | e^{j\theta_{Z_F}})} \times Z_F \quad (2)$$

where: V_s and θ_{V_s} = the respective magnitude and phase angle of the stimulus voltage
 V_{Z_F} and θ_{Z_F} = the respective magnitude and phase angle of the voltage across the feedback impedance

Calculating the real part of Z_X will return the resistive component of the impedance while calculating the imaginary component will yield the inductive or capacitive reactance value. To minimize measurement errors at higher test frequencies, Z_F also needs to be treated as a complex number.

If the DUT is purely resistive, then the phase information is not required and Z can be replaced with R . Equation 2 reduces to:

$$R_X = \left[\frac{V_S}{V_{R_F}} \right] \times R_F \quad (3)$$

Equation 3 can be used to calculate an unknown resistor value by using a DC source voltage rather than an AC stimulus. However, when using DC rather than AC to measure a resistor value, care must be used to minimize any DC offsets and thermal EMFs from relays and dissimilar metal junctions in the stimulus, measurement, and guard paths because they can have a negative impact on the accuracy of the measurement.

Two- and Three-Terminal Measurements

The circuit configuration in Figure 1 is called a two-terminal or two-wire measurement because only source and measure connections are used. This arrangement rarely occurs on populated PCB assemblies because other components typically are connected to the device being tested. Guarding must be used to eliminate the negative effects of these other components.

Figure 2 shows a simplified circuit where the DUT (R_X) is connected to other components (R_A and R_B) and indicates how to connect guard terminals to isolate the DUT. For simplicity, these complex impedances now are shown as simple resistances in the figure. Wire terminal resistances R_S , R_M , and R_G also are shown. With no passive guard in place at node G, a current divider would be created between R_X and the series combination of R_A and R_B . As a result, current would flow through both parallel paths and an error in the measurement would occur.

 


Figure 2. Basic Guarded DUT Impedance Measurement Configuration

With the passive grounded guard G in place, R_A now is shunted across the low output impedance source, and R_B is placed across the op-amp V^- and V^+ input terminals. With

virtually no voltage present across the V- to V+ terminals, there is negligible current flow through R_B . Virtually all of the current flowing through R_X also flows through R_F , where the unknown device current is measured with meter M_1 .

Four- and Six-Terminal Measurements

Path resistances R_S , R_M , and R_G can degrade the accuracy of the measurement and may need to be compensated for with additional measurement terminals. For example, if R_A is a low-impedance device, then current will flow through it and through the non-zero parasitic guard resistance R_G . This current will create a voltage at node G that ultimately will force a current through node M and introduce an error in the measurement of the DUT current V_{RF}/R_F . The wire resistances R_S and R_M also will affect the measured value of R_X . The calculated measurement value of R_X that includes the error effects of residuals R_S , R_M , and R_G for **Figure 2** is shown in Equation 4:

$$R_{X_{calc}} = R_S + R_M + R_X \times \frac{R_A R_B + R_S R_B + R_M R_A + R_G (R_A + R_B)}{R_A R_B + R_G (R_A + R_B + R_X)} + R_M \times \frac{(R_A + R_B + R_X)}{R_A R_B + R_G (R_A + R_B + R_X)} \quad (4)$$

where: $R_{X_{calc}}$ = the calculated resistance value including measurement errors

R_S = the source lead resistance

R_M = the measurement lead resistance

R_X = the resistance being measured

R_G = the guard wire resistance

R_A = the Thevenin source-side guarded resistance

R_B = the Thevenin measurement-side guarded resistance²

Minimizing the guard error caused by the finite resistance R_G can be achieved by allowing the noninverting terminal of the op-amp input to sense the voltage at node G remotely. This configuration, shown in **Figure 3**, is what is commonly called a four-wire guarded measurement, not to be confused with a four-wire Kelvin measurement. With the addition of this fourth terminal, there typically will be negligible voltage across R_B and therefore negligible error current through R_M that would be injected into the transimpedance amplifier from node G.

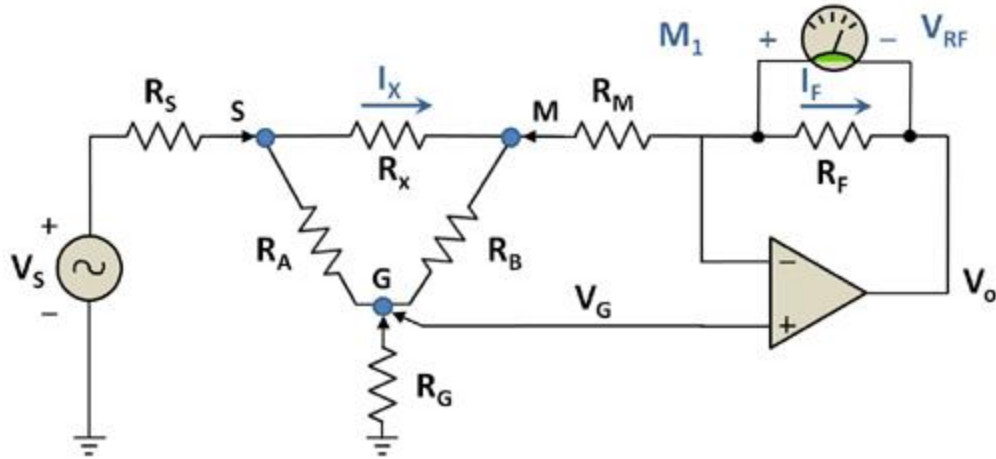


Figure 3. Guarded Measurement Configuration with Guard Voltage Sense

Adding another two terminals or wires can help to eliminate the errors caused by the source and measure wire resistances R_S and R_M . This six-wire metrology is illustrated in **Figure 4**. Two possible options to connect the op-amp's negative input terminal are represented by the single-pole, double-throw switch. In position L, the op-amp current sense terminal is in the local position while the R position denotes a remote sense position. If there is no need for guard terminal(s) or a guard sense terminal, the configuration will reduce to a classic four-wire Kelvin connection scheme that still will help mitigate the source and measure wire losses resulting from R_S and R_M .

 


Figure 4. Guarded Configuration with Guard Voltage Sense and Remote or Local Feedback

Referring again to Figure 4, the digitizer measurements can be made with two individual meters M_1 and M_2 that may have individual gain (K_1, K_2) and offset errors ($V_{\text{offset}1}, V_{\text{offset}2}$). These gain and offset terms, even if calibrated out, may drift over time and temperature, negatively affecting the measured value of R_X (Equation 5).

$$R_X = \left[\frac{V_{R_X} K_1 + V_{offset1}}{V_{R_F} K_2 + V_{offset2}} \right] \times R_F \quad (5)$$

However, if a single digitizer is used that is multiplexed between measuring the R_X voltage and the R_F voltage, the gain errors K_1 and K_2 tend to mathematically cancel because they are nearly the same value. Further, if the real and imaginary terms of the measurement are extracted through a single-bin discrete Fourier transform, then the DC offset terms can be eliminated from the measurement bin. Additionally, the impedance instrument can be designed to interleave alternating measurements of DUT voltage V_{R_X} and DUT current V_{R_F/R_F} within a single or multiple AC cycles, thereby adding no additional test time for the unit test period.

A plot of the percentage error as a function of the value of R_X for 3-wire, 4-wire, and 6-wire local and remote current sense measurements is illustrated in **Figure 5**. The conditions for this plot are $R_S = R_M = 0.8 \Omega$, $R_G = 0.4 \Omega$, and $R_A = R_B = 50 \Omega$. The error increase of the 3- and 4-wire measurements below about 200 Ω is caused by the series resistances R_S and R_M while the increase in the 3-wire plot above 200 Ω is a result of the combination of the guard voltage G and a low value of R_B that continues to inject error current into the current meter as the current from R_X is diminishing with increasing R_X values.

 


Figure 5. Measurement Error vs. Circuit Configuration

DUT Equivalent Circuits

Most in-circuit testers can return series and parallel equivalent circuits involving C_S , C_P , L_S , L_P , R_S , and R_P for a given impedance measurement. When measuring a capacitor with no physical series or parallel resistors in the circuit, it is sometimes not clear whether C_S or C_P should be used. The calculated values of C_S and C_P can be quite different because of the

quality of the component, the measurement path resistance, the component value, and the applied test frequency.

As a general rule of thumb, if the capacitor has a value less than 10 nF, C_p should be used because the parallel resistance is likely to have a more significant effect on the measurement than the series resistance. Above about 1 to 10 μ F, the parallel resistance is likely to have less effect than the series resistance, so C_s should be used in these instances. Similarly, low values of resistance generally should use R_s while high values should use R_p . Comparing the reactance of a capacitor or inductor to the parasitic resistance values can help in determining whether to use a series or a parallel model.

Other Test Considerations

When testing a component, it may not be clear which pin should be the source node and which pin should be the measurement node. The key to determining the best connections for the test is to consider what else is connected to the pins of the DUT. For example, if one lead of the DUT is connected to a super node such as a power or ground node, this lead should be placed on the source side rather than on the current meter's measurement pin. With a super node, many other nodes will need to be guarded and that will place a low-impedance and possibly highly capacitive load on the summing junction of the current meter.

A low value resistive load will lower the available loop gain of the amplifier and create a measurement error. A capacitive load will create an open-loop pole in the feedback network and degrade the phase margin of the op-amp and can cause excessive ringing and possible oscillation. In general, any large-value capacitors on a component lead or low-value resistors should be placed on the source node rather than the measure node.

It is possible for a measurement to return a negative value. The most common reason for this is that a large capacitance is being guarded on the measurement node. This guarded capacitor, when combined with the op-amp feedback resistor, creates an open-loop pole in the feedback network, thereby degrading the phase margin of the op-amp. In the closed-loop response of the measurement amplifier, there will be amplitude peaking and a large phase change.

If the test frequency is higher than the peaking frequency, then the calculated capacitor or resistor value will likely be negative. Operating at a test frequency below the peaking point or lowering the feedback resistance value should rectify the problem at the expense of some loss in overall measurement accuracy. The approximate peaking frequency is given in Equation 6:³

$$F_{peak} \approx \sqrt{A_{vo} F_{P_1} F_{P_2}} \quad (6)$$

where: F_{P1} = open-loop pole of op-amp

$$F_{P_2} = \frac{1}{2\pi R_F C_G}$$

A_{vo} = op-amp DC open-loop gain

Summary

ICT has been the workhorse of the manufacturing industry for more than 40 years and still is the most economical way to identify the largest range of process and component defects on the manufacturing line. Analog testing of passive components is as important as ever because of their increased usage. Understanding the principles behind analog testing is invaluable in generating stable tests that can hold up to high-volume PCB manufacturing.

References

1. *TestStation Testing Theory*, Teradyne, Number 034-324, April, 2006.
2. Khazam, M., "Predicting Test Accuracy for Analog In-Circuit Testing," *Proceedings of the International Test Conference*, IEEE, 1983, Paper 20.1.
3. Suto, A. J., *ACZ High Guard Calculations*, GenRad, Application Note, 1996.

Acknowledgements

Hall, H. P., *Multi-Terminal Impedance Measurements, or...Why Do those New Bridges Use So Many Connections?*, GenRad, Application Note Form JN 4166A, 1980.

About the Author

Anthony Suto is a senior staff scientist at Teradyne and has more than 32 years of design experience in the automatic test and inspection equipment industry. Suto received his electrical engineering degree from Union College in New York and has authored a variety of patents and technical papers. anthony.suto@teradyne.com

Published in December 2012 issue of Evaluation Engineering